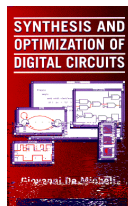


Timing Issues in Multi-level Logic Optimization

Giovanni De Micheli
Integrated Systems Centre
EPF Lausanne



This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

Module 1

◆ Objectives:

- ◆ Timing verification:
- ◆ Delay modeling
- ◆ Critical paths
- ◆ The false path problem

Timing verification and optimization

◆ Verification:

- ◆ Check that a circuit runs at speed
 - ◆ Satisfies I/O delay constraints
 - ◆ Satisfies cycle-time constraints

◆ Optimization:

- ◆ Minimum *delay*
 - ◆ (subject to *area* constraints)
- ◆ Minimum *area*
 - ◆ Subject to *delay* constraints

Delay modeling

◆ Gate delay modeling:

- ◆ Straightforward for bound networks
- ◆ Approximations for unbound networks

◆ Network delay modeling:

- ◆ Compute signal propagation
 - ◆ Topological methods
 - ◆ Logic/topological methods (false paths)

Gate delay modeling unbound networks

◆ Virtual gates:

- ◆ Logical expressions

◆ Stage delay model:

- ◆ Unit delay per vertex


◆ Refined models:

- ◆ Depending on fanout

Network delay modeling

- ◆ For each vertex v_i
- ◆ Propagation *delay* d_i :
 - ◆ I/O propagation delays are usually zero
- ◆ *Data-ready time* t_i :
 - ◆ Input data-ready time denote when inputs are available
 - ◆ Computed elsewhere by *forward traversal*
 - ◆ $t_i = d_i + \max_j t_j \quad \text{s.t. } (v_j, v_i) \in E$

Example

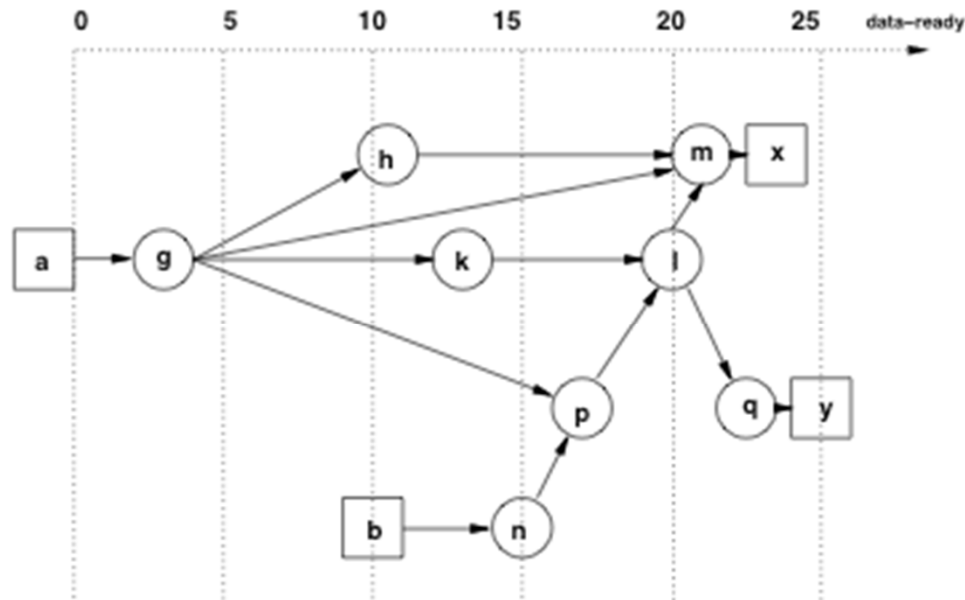

◆ Propagation delays:

- ◆ $d_g = 3$; $d_h = 8$; $d_m = 1$; $d_k = 10$; $d_l = 3$
- ◆ $d_n = 5$; $d_p = 2$; $d_o = 2$; $d_x = 2$; $d_y = 3$

Network delay modeling

◆ For each vertex v_i :


◆ Required *data-ready time* \underline{t}_i :

- ◆ Specified at the primary outputs
- ◆ Computed elsewhere by *backward traversal*
- ◆ $\underline{t}_i = \min_j \underline{t}_j - d_j \text{ s.t. } (v_i, v_j) \in E$

◆ Slack s_i :

- ◆ Difference between required and actual data-ready times
- $$s_i = \underline{t}_i - t_i$$

Example

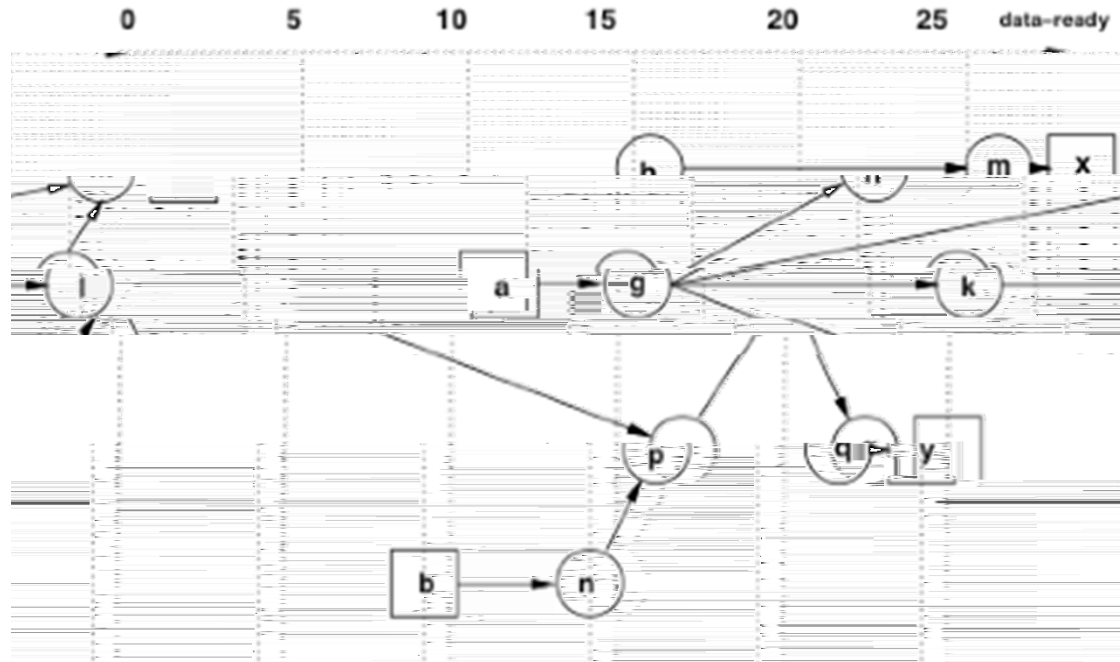


◆ Required data-ready times:


- ◆ $t_x = 25$ and $t_y = 25$

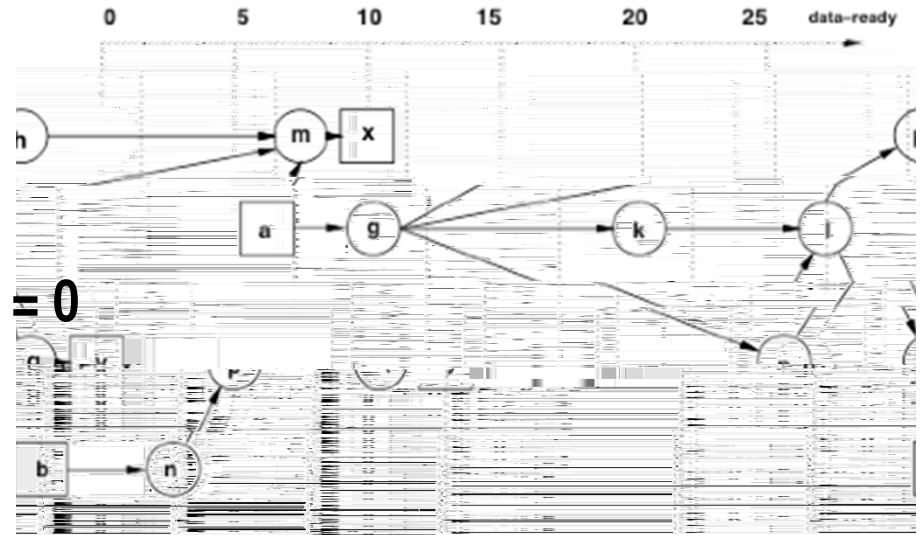Example

- ◆ $s_x = 2; s_y = 0$
- ◆ $\underline{t}_m = 25 - 2 = 23; s_m = 23 - 21 = 2$
- ◆ $\underline{t}_q = 25 - 2 = 22; s_q = 22 - 22 = 0$
- ◆ $\underline{t}_l = \min \{23 - 1; 22 - 2\} = 20; s_l = 20 - 20 = 0$
- ◆ $\underline{t}_b = 23 - 1 = 22; s_h = 22 - 11 = 11$
- ◆ $\underline{t}_k = 20 - 3 = 17; s_k = 17 - 13 = 4$
- ◆ $\underline{t}_p = 20 - 3 = 17; s_p = 17 - 17 = 0$
- ◆ $\underline{t}_n = 17 - 2 = 15; s_n = 15 - 15 = 0$
- ◆ $\underline{t}_b = 15 - 5 = 10; s_b = 10 - 10 = 0$
- ◆ $\underline{t}_g = \min \{22 - 11; 17 - 10; 17 - 2\} = 7; s_g = 7 - 3 = 4$
- ◆ $\underline{t}_a = 7 - 3 = 4; s_a = 4 - 0 = 4$



Example

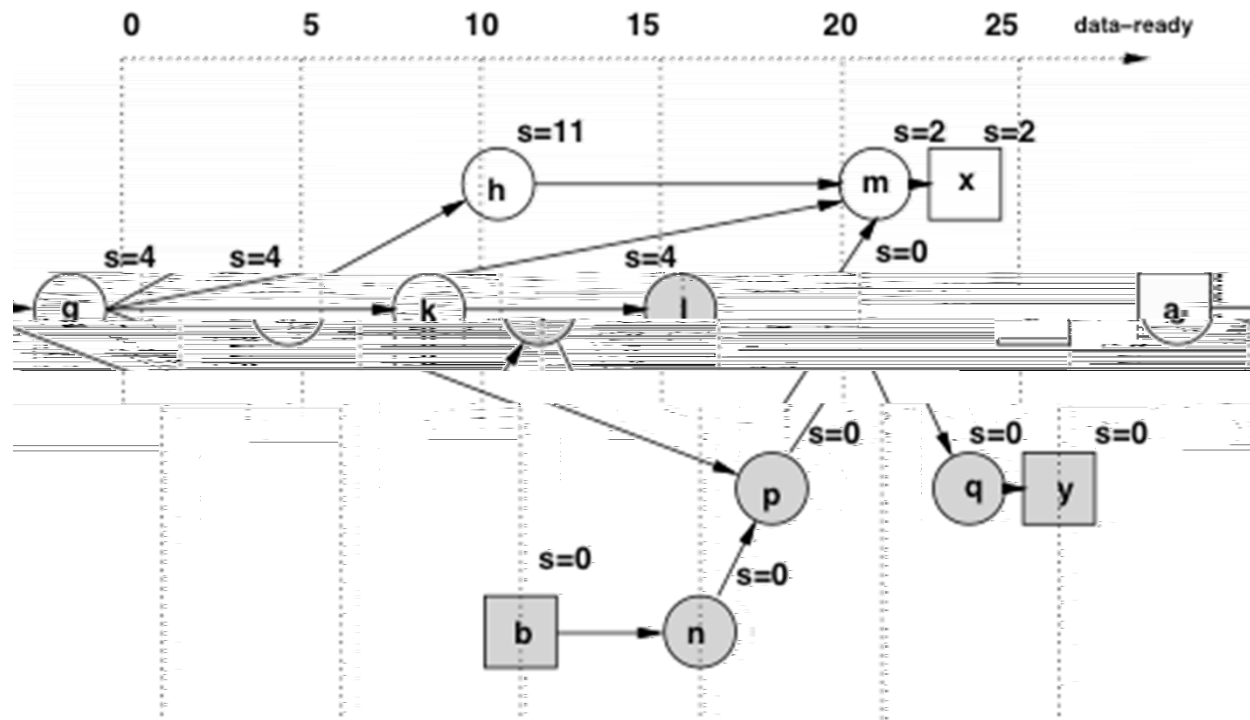

Topological critical path

◆ Assume topologic computation of :

- ◆ Data-ready by forward traversal
- ◆ Required data-ready by backward traversal


◆ *Topological critical path* :

- ◆ Input/output path with zero slacks
- ◆ Any increase in the vertex propagation delay affects the output data-ready time

◆ A topological critical path may be *false*:

- ◆ No event can propagate along that path

Example

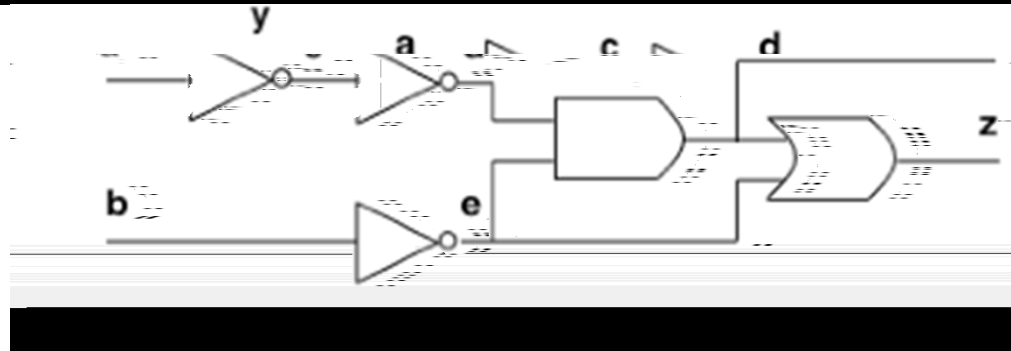

- ◆ All gates have unit delay
- ◆ All inputs ready at time 0
- ◆ Longest topological path : $(v_a, v_c, v_d, v_y, v_z)$:
 - ◆ Path delay: 4 units
- ◆ Critical true path: (v_a, v_c, v_d, v_y) :
 - ◆ Path delay: 3 units

Sensitizable paths



Sensitizable paths

◆ Path:

- ◆ Ordered set of vertices

◆ Inputs to a vertex:

- ◆ Direct predecessors

◆ Side-inputs of a vertex:

- ◆ Inputs not on the path

Dynamic sensitization condition

◆ Path: $P = (v_{xo}, v_{x1}, \dots, v_{xm})$


◆ An event propagates along P if :

$$\partial f_{xi} / \partial x_{i-1} = 1, i = 1, 2, \dots, m$$

◆ Remarks :

- ◆ Boolean differences are function of the side-inputs and values on the side-inputs may change
- ◆ Boolean differences must be true *at the time that the event propagates*

Example

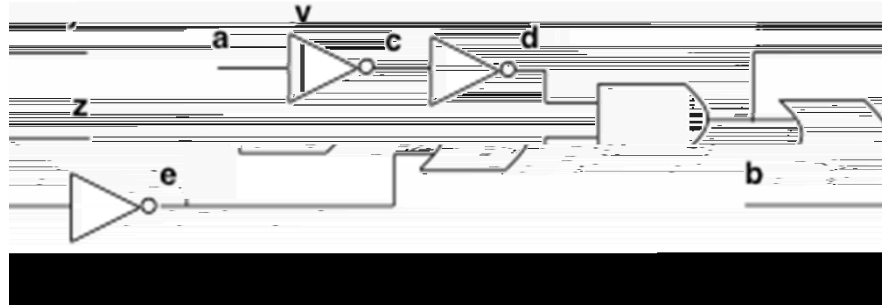

◆ Path: $(V_a, V_c, V_d, V_y, V_z)$

- ◆ $\partial f_y / \partial d = e = 1$ at time 2
- ◆ $\partial f_x / \partial y = e' = 1$ at time 3

◆ Not dynamically sensitizable because **e** settles at time 1


Static sensitization

- ◆ Simpler, weaker model
- ◆ We neglect the requirement on *when* the Boolean differences must be true to propagate an event
- ◆ There is an assignment of primary inputs **c** such that:

$$\partial f_{x_i}(\mathbf{c}) / \partial x_{i-1} = 1 \quad i=1,2, \dots, m$$

- ◆ May lead to *underestimate* delays

Example

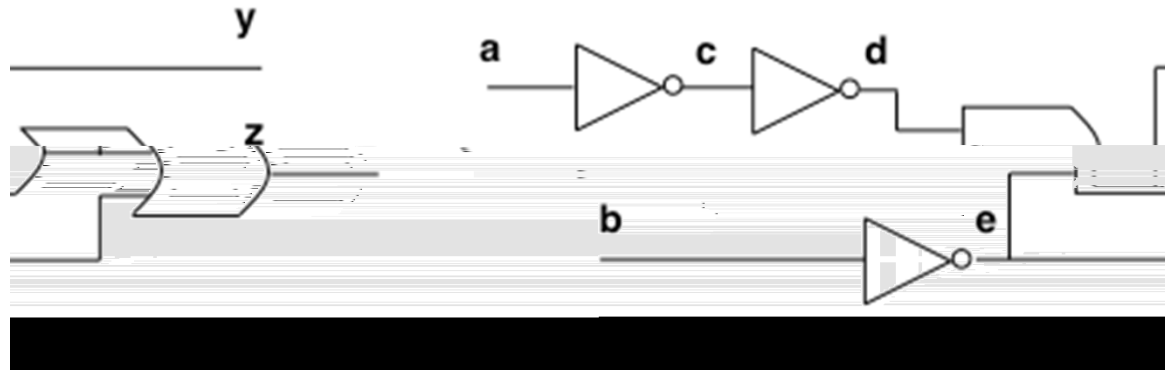

◆ Not statically sensitizable

Example

◆ All gates have unit delay

◆ Topological critical paths:


- ◆ $\{(V_a, V_d, V_g, V_o); (V_b, V_d, V_g, V_o)\}$
- ◆ Path delay : 3
- ◆ Not statically sensitizable

◆ Other path:

- ◆ (V_a, V_e, V_o)
- ◆ Path delay: 2

◆ Assume:

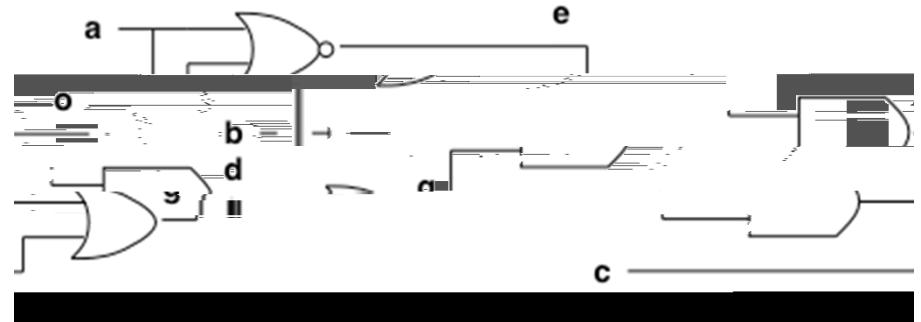- ◆ $c = 0$ and a, b dropping from 1 to 0
- ◆ Event propagates to output !!!



Modes for delay computation

◆ Transition *mode*:

- ◆ Variables assumed to hold previous values
 - ◆ Model circuit node capacitances
- ◆ *Two test vectors* are needed

◆ Floating *mode*:

- ◆ Circuit is assumed to be memoryless
 - ◆ Variables have unknown value until set by input test vector
- ◆ Need *only one* test vector

Modes for delay computation

- ◆ ***Floating mode*** delay computation is simpler than *transition mode* computation
- ◆ ***Floating mode*** is a pessimistic approach
- ◆ ***Floating mode*** is more robust:
 - ◆ *Transition mode* may not have the *monotone speed-up* property

Monotone speed-up property


◆ Propagation delays are upper bounds:

- ◆ What happens if gates are *faster* than expected?

◆ We must insure that speeding-up a gate does not slow-down the circuit:

- ◆ Topological critical paths are robust
- ◆ What about dynamically sensitizable paths in transition mode?

Example

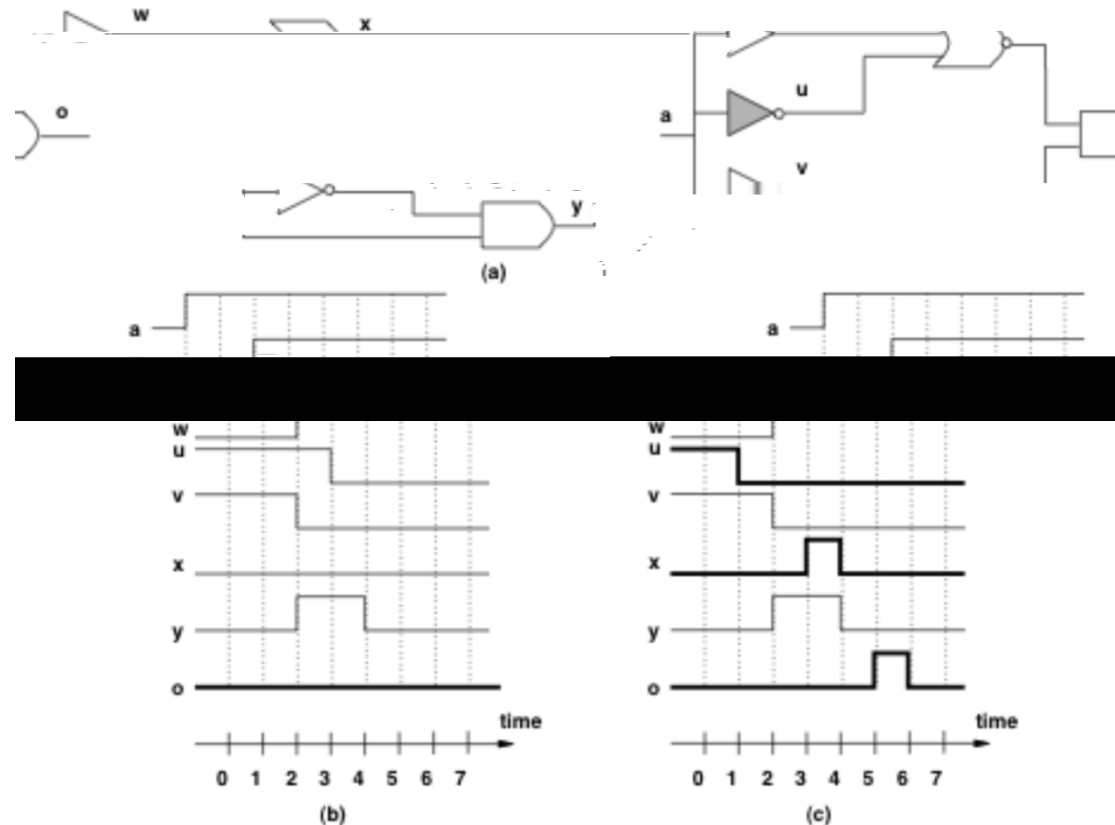

- ◆ Propagation delay: 2 units
- ◆ Shaded gate: 3 units and 1 unit

Static co-sensitization

◆ Assumption:

- ◆ Circuit modeled by *AND*, *OR*, *INV* gates
- ◆ *INV* are irrelevant to the analysis
- ◆ Floating mode

◆ Controlling values:

- ◆ 0 for *AND* gate
- ◆ 1 for *OR* gate

◆ Gate has *controlled value*

Static co-sensitization


- ◆ Path: $P = (v_{x0}, v_{x1}, \dots, v_{xm})$
- ◆ A vector *statically co-sensitizes* a path to 1 (or to 0) if :
 - ◆ $x_m = 1$ (or 0) and
 - ◆ v_{xi-1} has a controlling value whenever v_{xi} has a controlled value
- ◆ Necessary condition for a path to be true

False path detection test

◆ For all input vectors, one of the following is true:

- ◆ (1) A gate is controlled and
 - ◆ the path provides a non-controlling value
 - ◆ a side-input provides a controlling value
- ◆ (2) A gate is controlled and
 - ◆ The path and a side-input have controlling values
 - ◆ The side-input presents the controlling value first
- ◆ (3) A gate is not controlled and
 - ◆ A side-input presents the non-controlling value last

Example

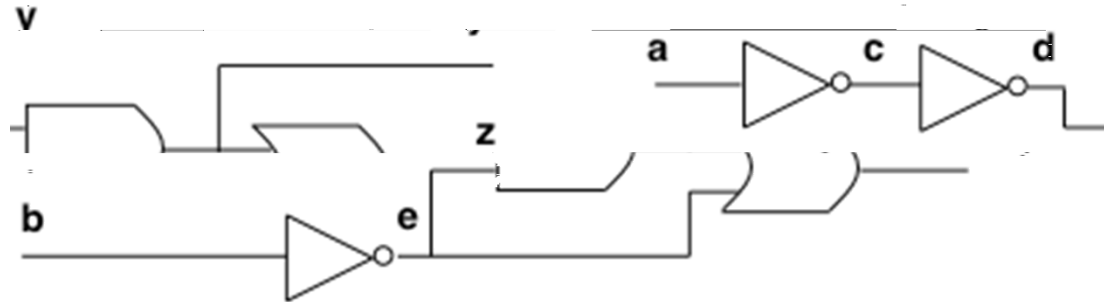

◆ Path: $(v_a, v_c, v_d, v_y, v_z)$

◆ For $a = 0, b = 0$:

- ◆ Condition (1) occurs at the OR gate

◆ For $a = 0, b = 1$:

- ◆ Condition (2) occurs at the AND gate

◆ For $a = 1, b = 0$:

- ◆ Condition (2) occurs at the OR gate

◆ For $a = 1, b = 1$:

- ◆ Condition (1) occurs at the AND gate

Important problems

- ◆ Check if circuit works at speed \underline{t} :
 - ◆ Verify that all true paths are faster than \underline{t}
 - ◆ Show that all paths slower than \underline{t} are false
- ◆ Compute groups of false paths
- ◆ Compute critical true path:
 - ◆ Binary search for values of \underline{t}
 - ◆ Show that all paths slower than \underline{t} are false

Module 2

◆ Objectives:

- ◆ Algorithms for timing optimization
- ◆ Favorable logic transformations

Algorithms for delay minimization

◆ Alternate:

- ◆ Critical path computation
- ◆ Logic transformation on critical vertices

◆ Consider *quasi critical paths*:

- ◆ Paths with near-critical delay
- ◆ Small slacks

Algorithms for delay minimization

◆ REDUCE_DELAY ($G_n(V,E)$, ε) {

repeat {

- ◆ Compute critical paths and critical delay τ
- ◆ Set output required data-ready times to τ
- ◆ Compute slacks
- ◆ U = vertex subset with slack lower than ε
- ◆ W = select vertices in U
- ◆ Apply transformations to vertices W
- ◆ } *until* (no transformation can reduce τ)

}

Transformation for delay reduction


- ◆ Reduce propagation delay
- ◆ Reduce dependencies from critical inputs
- ◆ *Favorable* transformation:
 - ◆ Reduces local data-ready time
 - ◆ Any data-ready time increase at other vertices is bounded by the local slack

Example

- ◆ **Unit gate delay**
- ◆ **Transformation:**
 - ◆ **Elimination**
- ◆ **Always favorable**
- ◆ **Obtain several area/delay trade-off points**

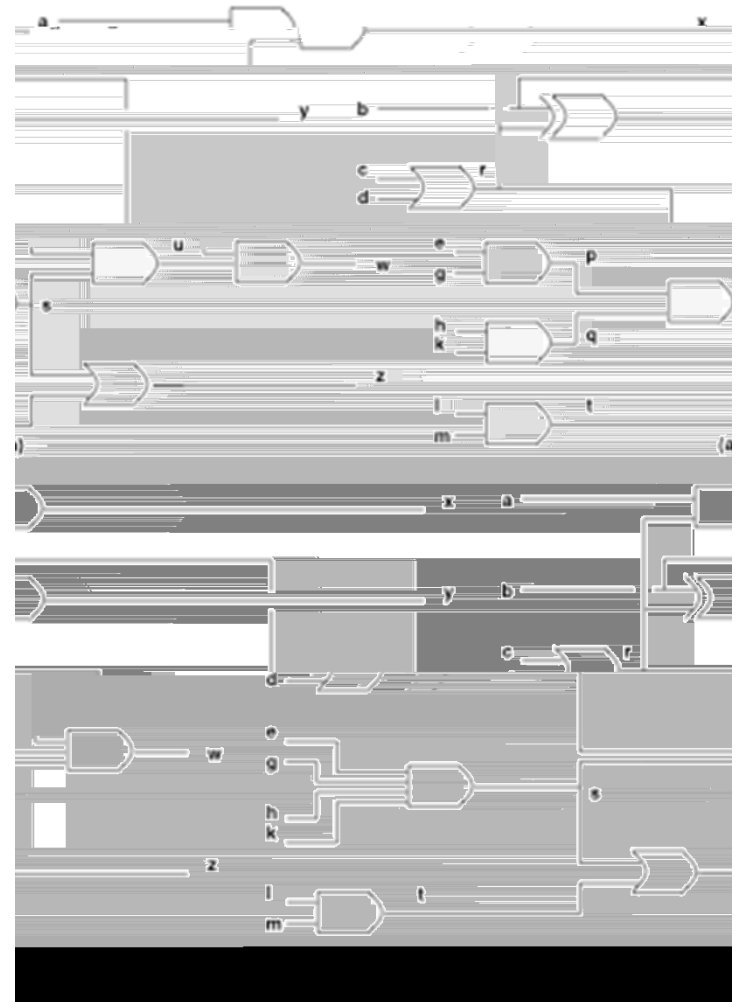Example

- ◆ Iteration 1:
eliminate v_p, v_q . (No literal increase)
- ◆ Iteration 2:
eliminate v_u . (No literal increase)
- ◆ Iteration 3:
eliminate v_r, v_s, v_t . (Literal increase)



More refined delay models


◆ Elimination:

- ◆ Reduces one stage
- ◆ Yields more complex and slower gates
- ◆ May slow other paths

◆ Substitution:

- ◆ Adds one dependency
- ◆ Loads and slows a gate
- ◆ May slow other paths

Example

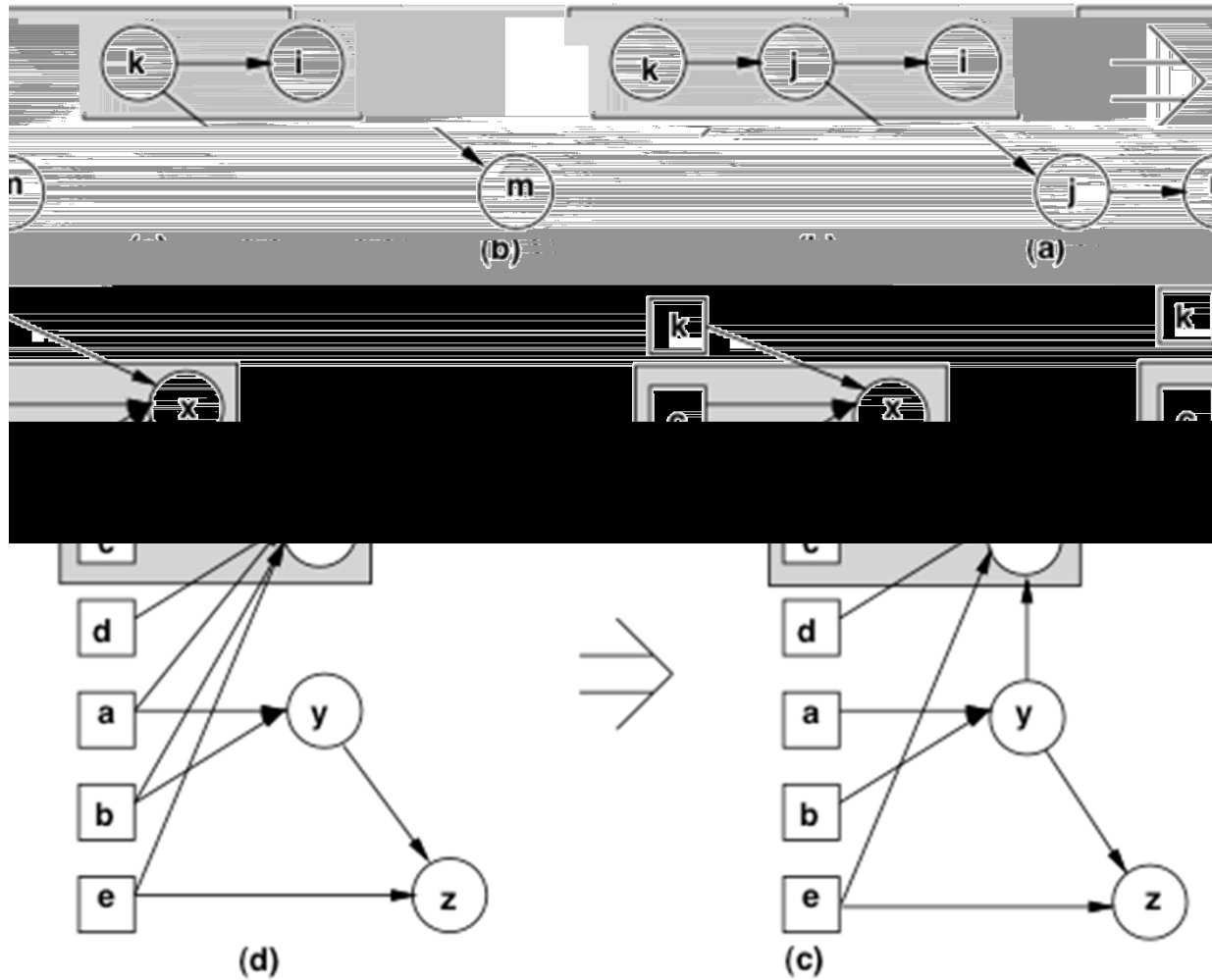


Speed-up algorithm

- ◆ Determine a subnetwork W of depth d
- ◆ Collapse subnetwork by elimination
- ◆ Duplicate vertices with successors outside W :
 - ◆ Record *area penalty*
- ◆ Resynthesize W by timing-driven decomposition
- ◆ Heuristics:
 - ◆ Choice of W
 - ◆ Monitor *area penalty* and *potential speed-up*

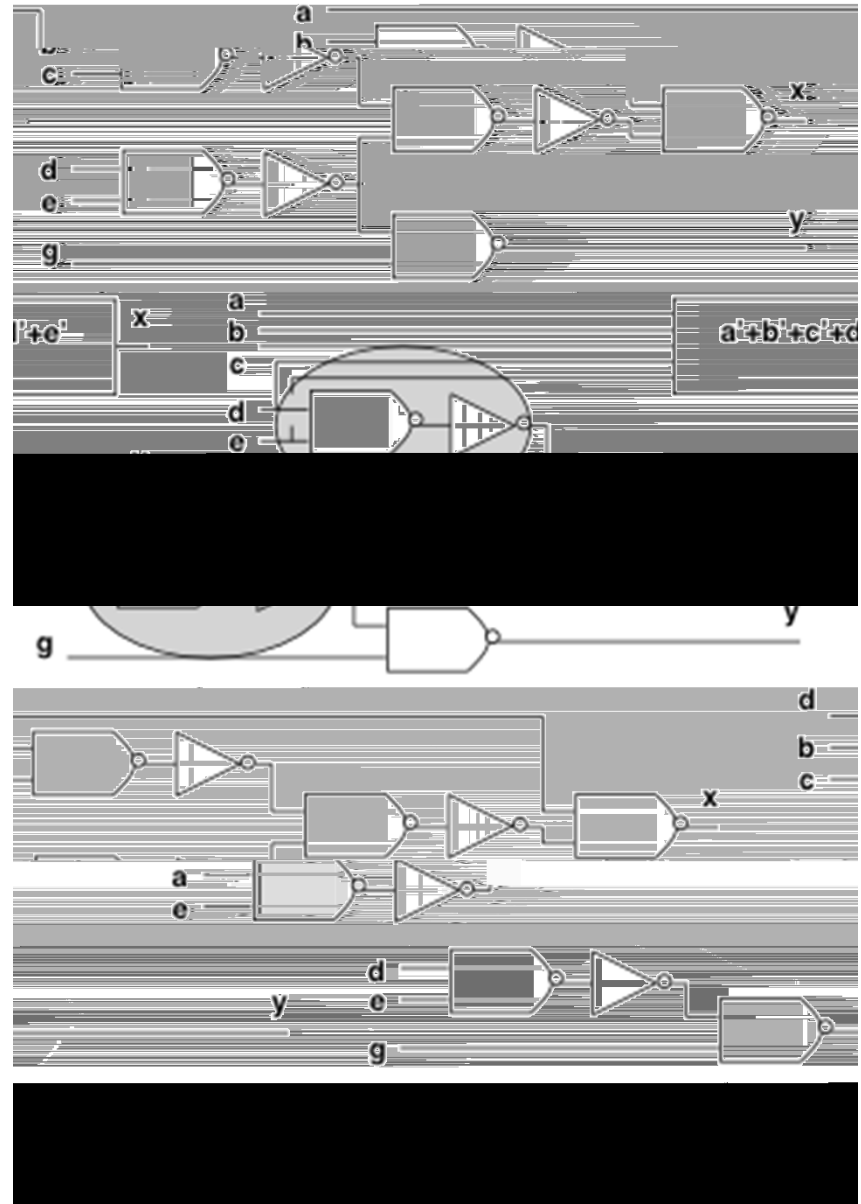Example

- ◆ NAND delay = 2
INV delay = 1
- ◆ All input data-ready are 0, except = $t_d = 3$



Minimal-area synthesis under delay constraints

- ◆ **Start from timing-feasible network**
- ◆ ***Minimize area* while preserving timing feasibility:**
 - ◆ Use area optimization algorithms
 - ◆ Monitor delays and slacks
 - ◆ Reject transformations yielding negative slacks

Making a network timing feasible

◆ Naive approach:



- ◆ Mark vertices with negative slacks
- ◆ Apply transformations to marked vertices

◆ Redefined approach:

- ◆ Transform multiple I/O delay constraints into single constraint by delay padding
- ◆ Apply algorithms for CP minimization
- ◆ Stop when constraints are satisfied

Example

$$\bar{t} = [2332]^T$$

 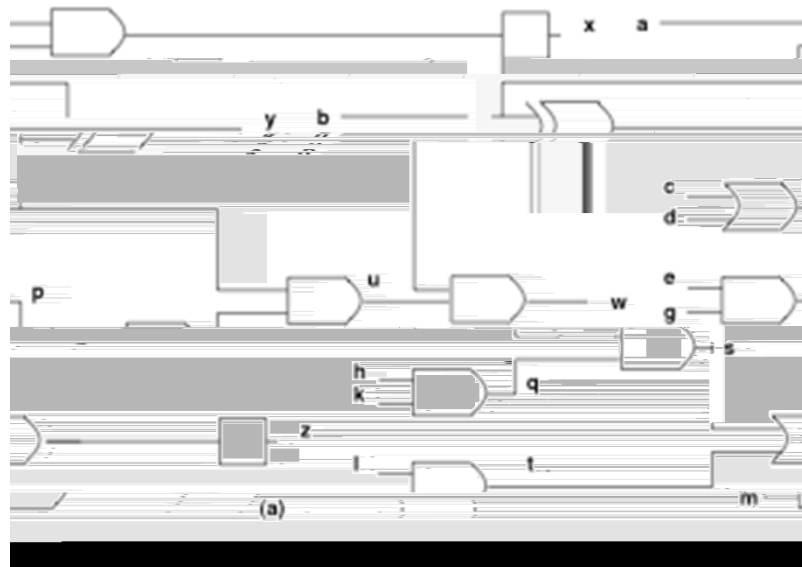

Summary

- ◆ **Timing optimization is crucial for achieving competitive logic design**
- ◆ **Timing optimization problems are hard:**
 - ◆ **Detection of critical paths**
 - ◆ **Elimination of false paths**
 - ◆ **Network transformations**